

Problems

Section 10.2 Nodal Analysis

10.1 Determine i in the circuit of Fig. 10.50.

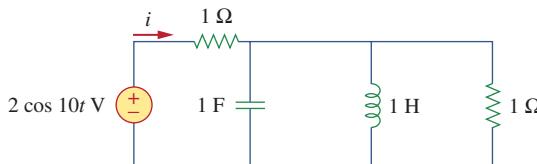


Figure 10.50

For Prob. 10.1.

10.2 Using Fig. 10.51, design a problem to help other **e2d** students better understand nodal analysis.

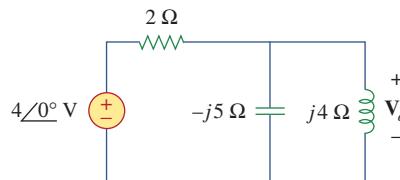


Figure 10.51

For Prob. 10.2.

10.3 Determine v_o in the circuit of Fig. 10.52.

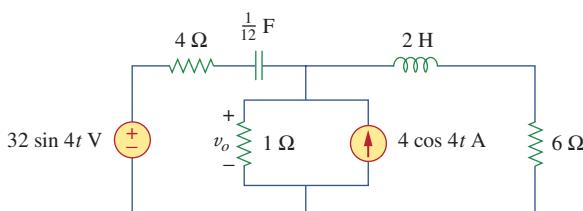


Figure 10.52

For Prob. 10.3.

10.4 Determine i_1 in the circuit of Fig. 10.53.

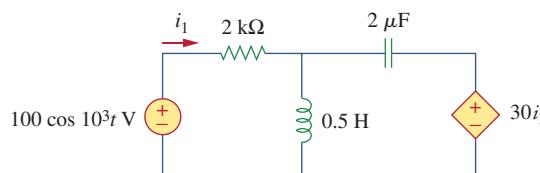


Figure 10.53

For Prob. 10.4.

10.5 Find i_o in the circuit of Fig. 10.54.

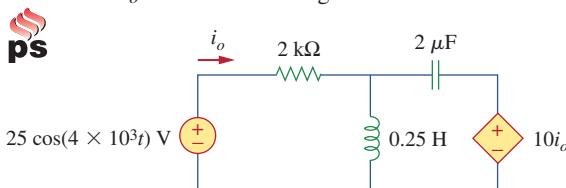


Figure 10.54

For Prob. 10.5.

10.6 Determine \mathbf{V}_x in Fig. 10.55.

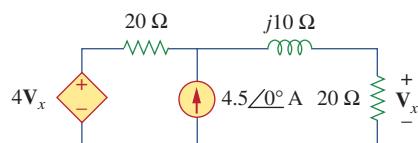


Figure 10.55

For Prob. 10.6.

10.7 Use nodal analysis to find \mathbf{V} in the circuit of Fig. 10.56.

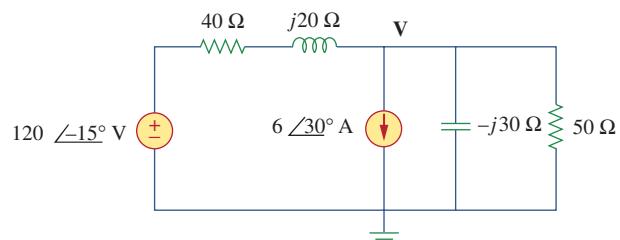


Figure 10.56

For Prob. 10.7.

10.8 Use nodal analysis to find current i_o in the circuit of Fig. 10.57. Let $i_s = 6 \cos(200t + 15^\circ)$ A. **ps ML**

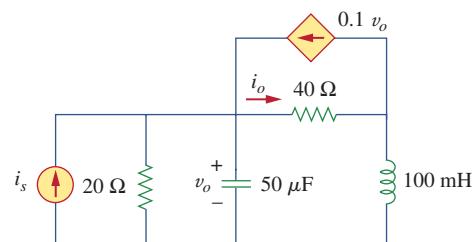


Figure 10.57

For Prob. 10.8.

10.9 Use nodal analysis to find v_o in the circuit of Fig. 10.58. **ps ML**


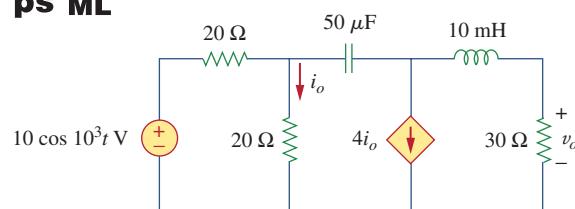


Figure 10.58


For Prob. 10.9.

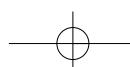

444


Chapter 10 Sinusoidal Steady-State Analysis

- 10.10** Use nodal analysis to find v_o in the circuit of Fig. 10.59. Let $\omega = 2$ krad/s.
ps ML

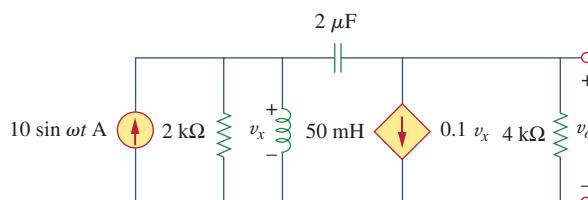**Figure 10.59**


For Prob. 10.10.

- 10.11** Apply nodal analysis to the circuit in Fig. 10.60 and determine I_o .
ps ML

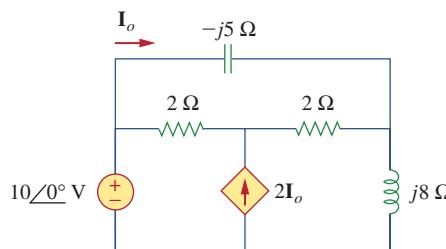**Figure 10.60**


For Prob. 10.11.

- 10.12** Using Fig. 10.61, design a problem to help other **end** students better understand nodal analysis.

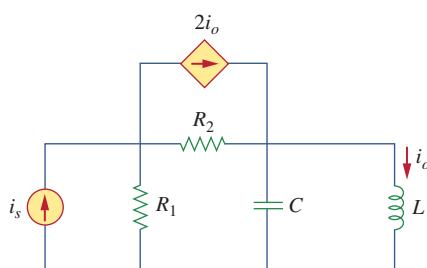**Figure 10.61**


For Prob. 10.12.

- 10.13** Determine V_x in the circuit of Fig. 10.62 using any method of your choice.
ps ML

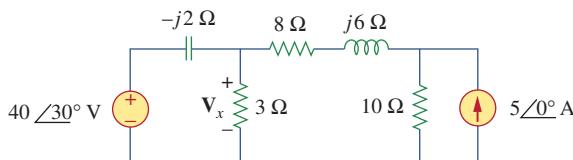**Figure 10.62**


For Prob. 10.13.

- 10.14** Calculate the voltage at nodes 1 and 2 in the circuit of Fig. 10.63 using nodal analysis.
ps ML

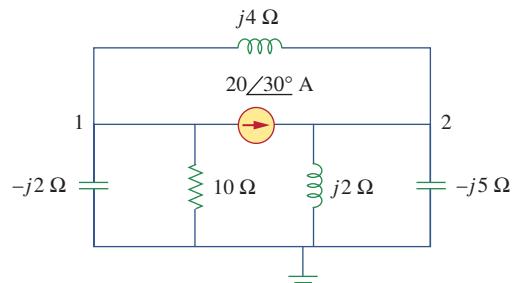**Figure 10.63**


For Prob. 10.14.

- 10.15** Solve for the current I in the circuit of Fig. 10.64 using nodal analysis.
ps ML

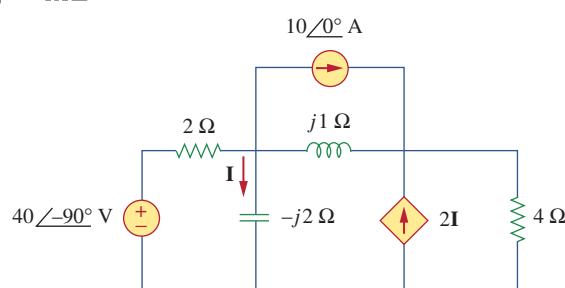**Figure 10.64**


For Prob. 10.15.

- 10.16** Use nodal analysis to find V_x in the circuit shown in Fig. 10.65.
ps ML

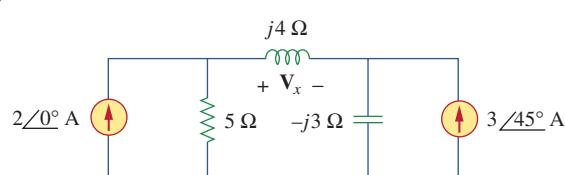
**Figure 10.65**

For Prob. 10.16.

- 10.17** By nodal analysis, obtain current I_o in the circuit of Fig. 10.66.
ps ML

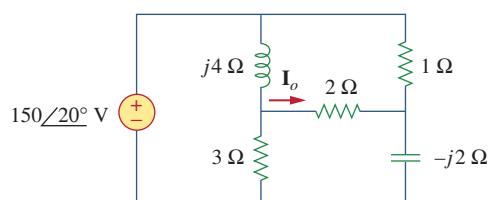**Figure 10.66**

For Prob. 10.17.

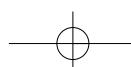

10.18 Use nodal analysis to obtain \mathbf{V}_o in the circuit of Fig. 10.67 below.

ps ML

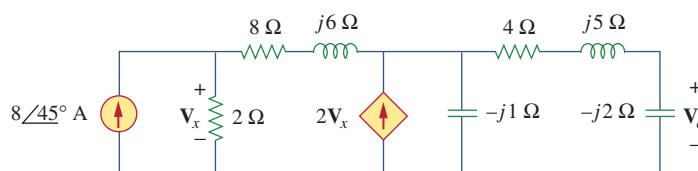


Figure 10.67

For Prob. 10.18.

10.19 Obtain \mathbf{V}_o in Fig. 10.68 using nodal analysis.

ps ML

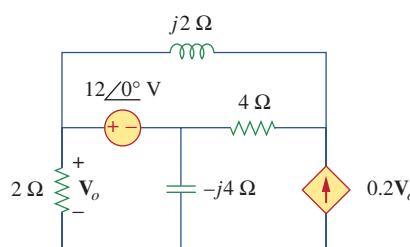


Figure 10.68

For Prob. 10.19.

10.20 Refer to Fig. 10.69. If $v_s(t) = V_m \sin \omega t$ and $v_o(t) = A \sin(\omega t + \phi)$, derive the expressions for A and ϕ .

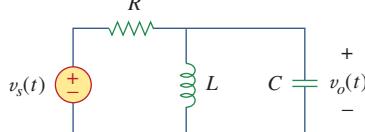


Figure 10.69

For Prob. 10.20.

10.21 For each of the circuits in Fig. 10.70, find $\mathbf{V}_o/\mathbf{V}_i$ for $\omega = 0$, $\omega \rightarrow \infty$, and $\omega^2 = 1/LC$.

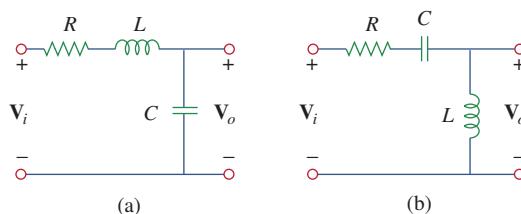


Figure 10.70

For Prob. 10.21.

10.22 For the circuit in Fig. 10.71, determine $\mathbf{V}_o/\mathbf{V}_s$.

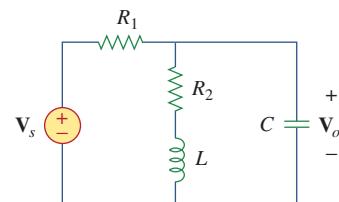


Figure 10.71

For Prob. 10.22.

10.23 Using nodal analysis obtain \mathbf{V} in the circuit of Fig. 10.72.

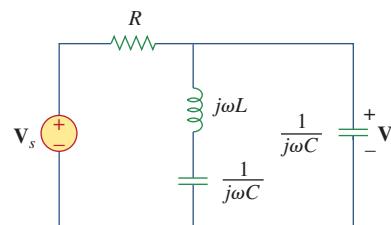


Figure 10.72

For Prob. 10.23.

Section 10.3 Mesh Analysis

10.24 Design a problem to help other students better understand mesh analysis.

ML

10.25 Solve for i_o in Fig. 10.73 using mesh analysis.


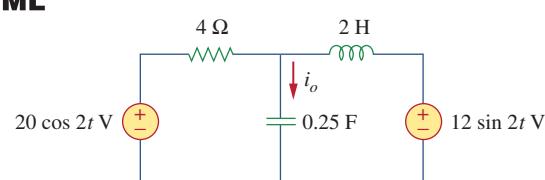


Figure 10.73


For Prob. 10.25.

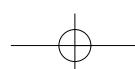

446


Chapter 10 Sinusoidal Steady-State Analysis

- 10.26** Use mesh analysis to find current i_o in the circuit of Fig. 10.74.

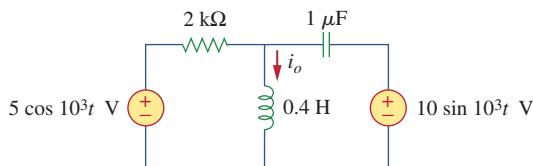**Figure 10.74**


For Prob. 10.26.

- 10.27** Using mesh analysis, find \mathbf{I}_1 and \mathbf{I}_2 in the circuit of Fig. 10.75.

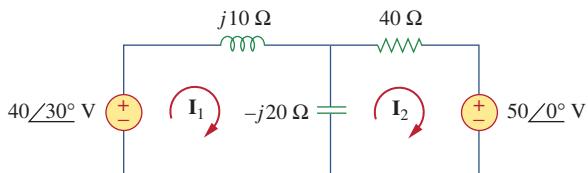ML**Figure 10.75**


For Prob. 10.27.

- 10.28** In the circuit of Fig. 10.76, determine the mesh currents i_1 and i_2 . Let $v_1 = 10 \cos 4t$ V and $v_2 = 20 \cos(4t - 30^\circ)$ V.

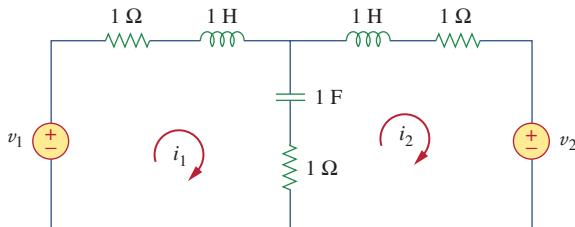**Figure 10.76**


For Prob. 10.28.

- 10.29** Using Fig. 10.77, design a problem to help other **end** students better understand mesh analysis.

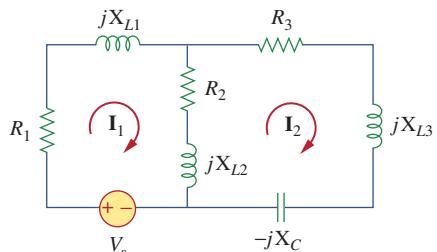
**Figure 10.77**

For Prob. 10.29.

- 10.30** Use mesh analysis to find v_o in the circuit of Fig. 10.78. Let $v_{s1} = 240 \cos(100t + 90^\circ)$ V, **ps** **ML** $v_{s2} = 160 \cos 100t$ V.

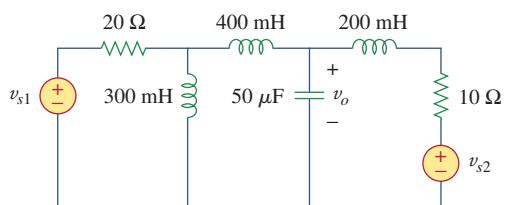
**Figure 10.78**

For Prob. 10.30.

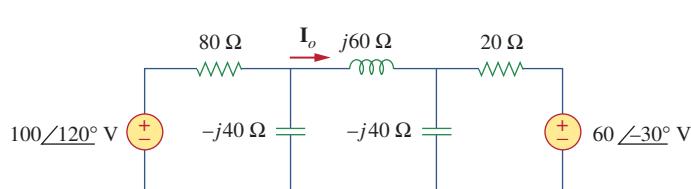
**Figure 10.79**

For Prob. 10.31.

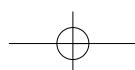- 10.31** Use mesh analysis to determine current \mathbf{I}_o in the **ps** **ML** circuit of Fig. 10.79 below.



- 10.32** Determine \mathbf{V}_o and \mathbf{I}_o in the circuit of Fig. 10.80 using mesh analysis.
ps ML

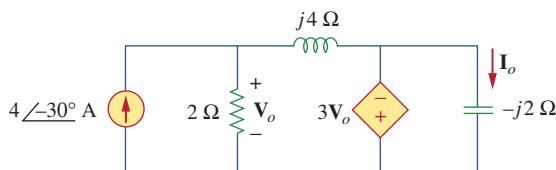**Figure 10.80**


For Prob. 10.32.

- 10.33** Compute \mathbf{I} in Prob. 10.15 using mesh analysis.
ps ML

- 10.34** Use mesh analysis to find \mathbf{I}_o in Fig. 10.28 (for Example 10.10).
ps ML


- 10.35** Calculate \mathbf{I}_o in Fig. 10.30 (for Practice Prob. 10.10) using mesh analysis.
ps ML

- 10.36** Compute \mathbf{V}_o in the circuit of Fig. 10.81 using mesh analysis.
ps ML

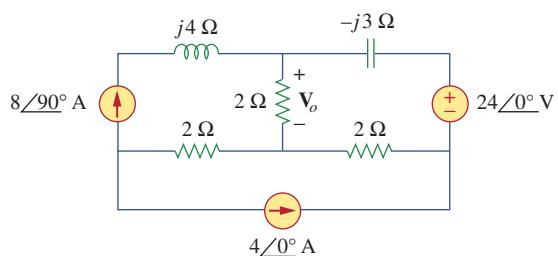**Figure 10.81**


For Prob. 10.36.

- 10.37** Use mesh analysis to find currents \mathbf{I}_1 , \mathbf{I}_2 , and \mathbf{I}_3 in the circuit of Fig. 10.82.
ps ML

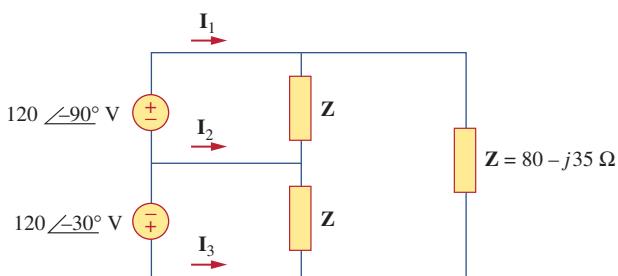**Figure 10.82**


For Prob. 10.37.

- 10.38** Using mesh analysis, obtain \mathbf{I}_o in the circuit shown in Fig. 10.83.
ps ML

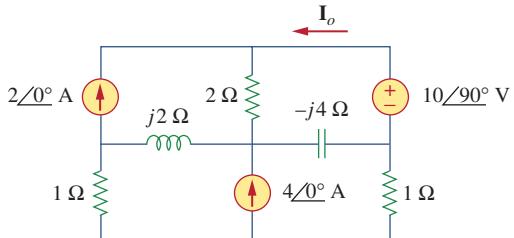**Figure 10.83**

For Prob. 10.38.


- 10.39** Find \mathbf{I}_1 , \mathbf{I}_2 , \mathbf{I}_3 , and \mathbf{I}_x in the circuit of Fig. 10.84.
ps ML

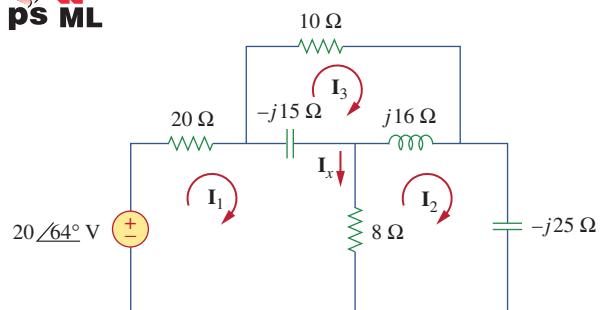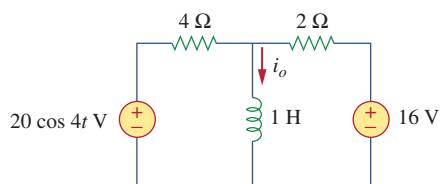**Figure 10.84**

For Prob. 10.39.


Section 10.4 Superposition Theorem

- 10.40** Find i_o in the circuit shown in Fig. 10.85 using superposition.


**Figure 10.85**

For Prob. 10.40.

- 10.41** Find v_o for the circuit in Fig. 10.86, assuming that $v_s = 3 \cos 2t + 8 \sin 4t$ V.

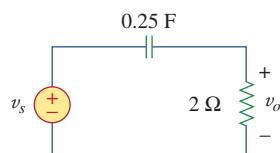**Figure 10.86**


For Prob. 10.41.

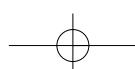

448


Chapter 10 Sinusoidal Steady-State Analysis

- 10.42** Using Fig. 10.87, design a problem to help other students better understand the superposition theorem.

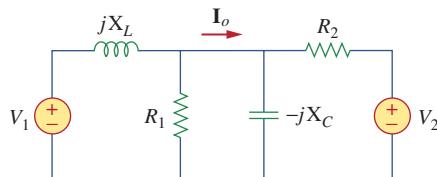**Figure 10.87**


For Prob. 10.42.

- 10.43** Using the superposition principle, find i_x in the circuit of Fig. 10.88.

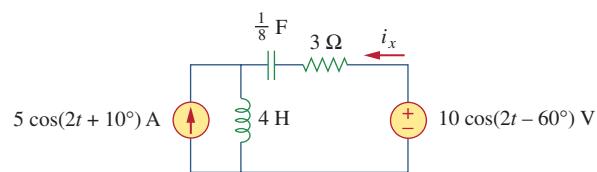**Figure 10.88**


For Prob. 10.43.

- 10.44** Use the superposition principle to obtain v_x in the circuit of Fig. 10.89. Let $v_s = 25 \sin 2t$ V and $i_s = 6 \cos(6t + 10^\circ)$ A.

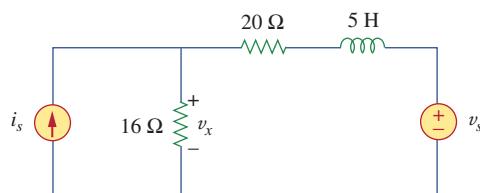**Figure 10.89**


For Prob. 10.44.

- 10.45** Use superposition to find $i(t)$ in the circuit of Fig. 10.90.

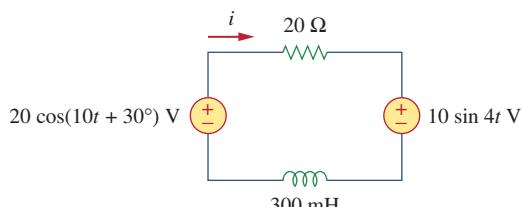**Figure 10.90**

For Prob. 10.45.


- 10.46** Solve for $v_o(t)$ in the circuit of Fig. 10.91 using the superposition principle.

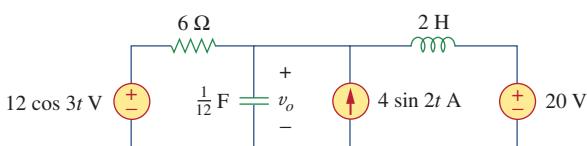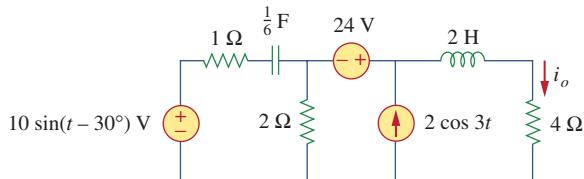**Figure 10.91**

For Prob. 10.46.

- 10.47** Determine i_o in the circuit of Fig. 10.92, using the superposition principle.

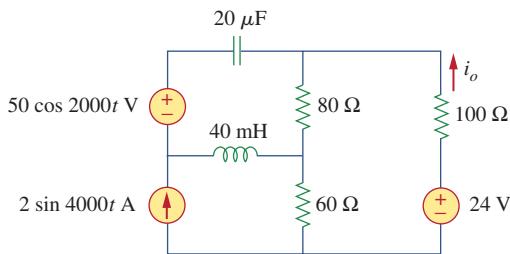
ps ML

**Figure 10.92**

For Prob. 10.47.

- 10.48** Find i_o in the circuit of Fig. 10.93 using superposition.

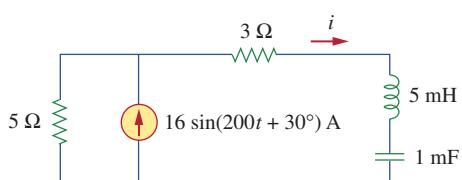
ps ML

**Figure 10.93**


For Prob. 10.48.

Section 10.5 Source Transformation


- 10.49** Using source transformation, find i in the circuit of Fig. 10.94.

**Figure 10.94**

For Prob. 10.49.

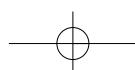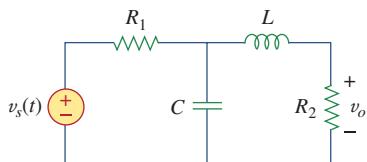

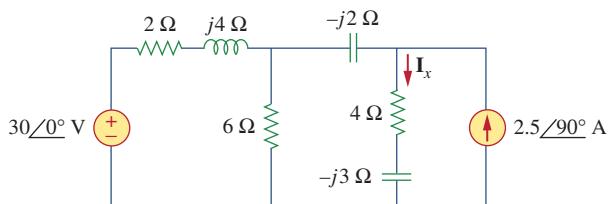
- 10.50** Using Fig. 10.95, design a problem to help other **end** students understand source transformation.

**Figure 10.95**

For Prob. 10.50.


- 10.51** Use source transformation to find \mathbf{I}_o in the circuit of Prob. 10.42.

- 10.52** Use the method of source transformation to find \mathbf{I}_x in the circuit of Fig. 10.96. **ps**

**Figure 10.96**

For Prob. 10.52.

- 10.53** Use the concept of source transformation to find \mathbf{V}_o in the circuit of Fig. 10.97. **ps**

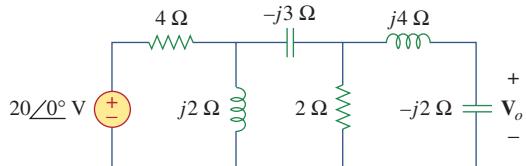
**Figure 10.97**

For Prob. 10.53.


- 10.54** Rework Prob. 10.7 using source transformation.

Section 10.6 Thevenin and Norton Equivalent Circuits

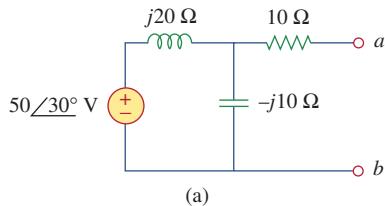- 10.55** Find the Thevenin and Norton equivalent circuits at terminals $a-b$ for each of the circuits in Fig. 10.98.



(a)

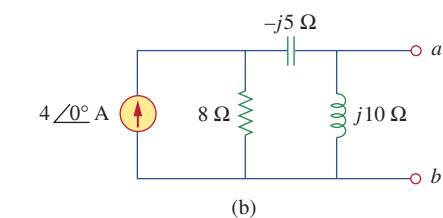


(b)


Figure 10.98

For Prob. 10.55.

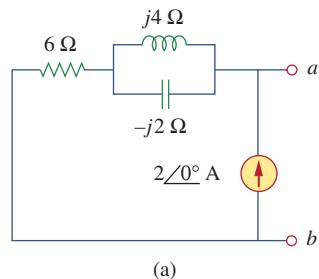- 10.56** For each of the circuits in Fig. 10.99, obtain Thevenin and Norton equivalent circuits at terminals $a-b$.



(a)

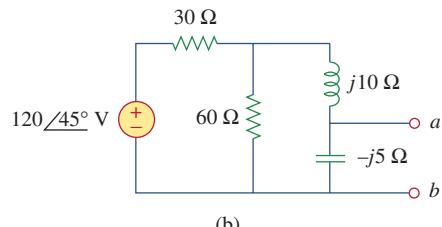


(b)

Figure 10.99


For Prob. 10.56.

- 10.57** Using Fig. 10.100, design a problem to help other **end** students better understand Thevenin and Norton equivalent circuits.

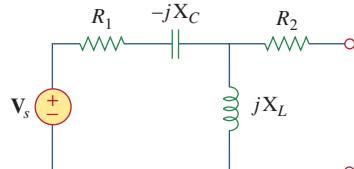
**Figure 10.100**

For Prob. 10.57.

- 10.58** For the circuit depicted in Fig. 10.101, find the Thevenin equivalent circuit at terminals $a-b$.

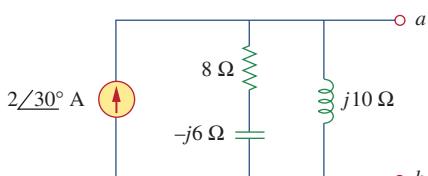**Figure 10.101**


For Prob. 10.58.

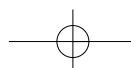

450


Chapter 10 Sinusoidal Steady-State Analysis

- 10.59** Calculate the output impedance of the circuit shown in Fig. 10.102.

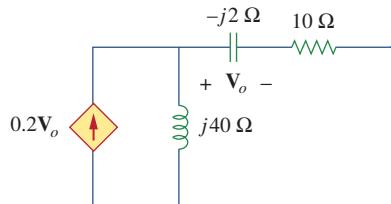**Figure 10.102**


For Prob. 10.59.

- 10.63** Obtain the Norton equivalent of the circuit depicted in Fig. 10.106 at terminals *a-b*.

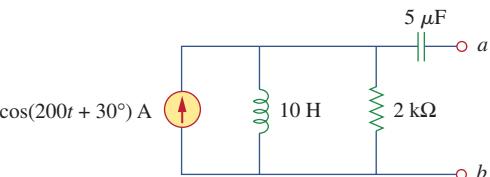in Fig. 10.106 at terminals *a-b*.**Figure 10.106**

For Prob. 10.63.


- 10.60** Find the Thevenin equivalent of the circuit in Fig. 10.103 as seen from:

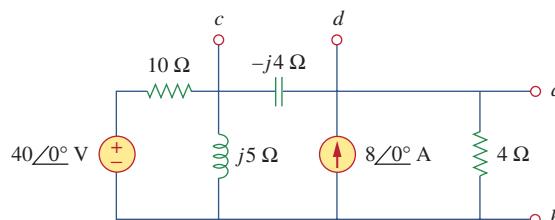(a) terminals *a-b* (b) terminals *c-d***Figure 10.103**

For Prob. 10.60.

- 10.61** Find the Thevenin equivalent at terminals *a-b* of the circuit in Fig. 10.104.


ps ML

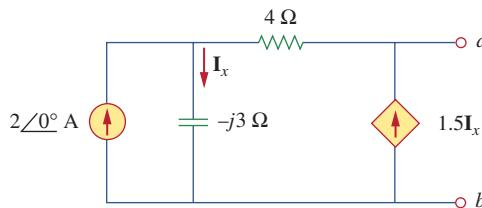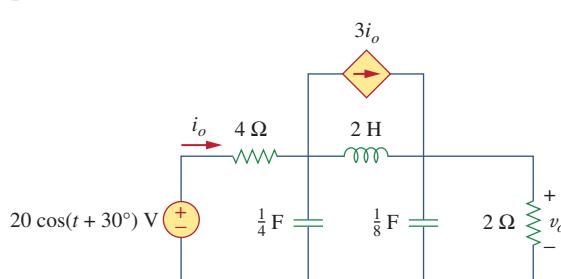**Figure 10.104**

For Prob. 10.61.


- 10.62** Using Thevenin's theorem, find v_o in the circuit of Fig. 10.105.

ps

**Figure 10.105**

For Prob. 10.62.


- 10.64** For the circuit shown in Fig. 10.107, find the Norton equivalent circuit at terminals *a-b*.

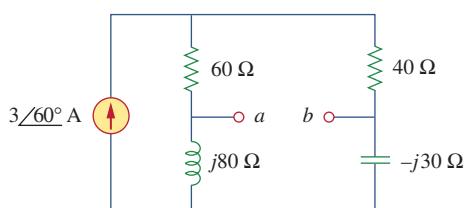equivalent circuit at terminals *a-b*.**Figure 10.107**

For Prob. 10.64.


- 10.65** Using Fig. 10.108, design a problem to help other students better understand Norton's theorem.

end

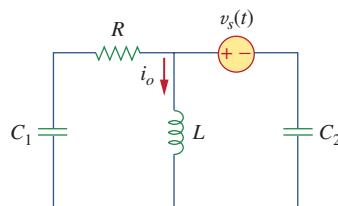
**Figure 10.108**


For Prob. 10.65.

- 10.66** At terminals *a-b*, obtain Thevenin and Norton equivalent circuits for the network depicted in Fig. 10.109. Take $\omega = 10$ rad/s.

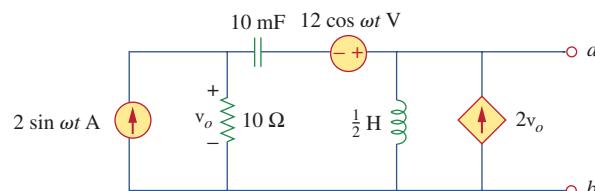
**Figure 10.109**

For Prob. 10.66.

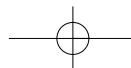

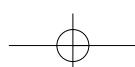


- 10.67** Find the Thevenin and Norton equivalent circuits at terminals *a-b* in the circuit of Fig. 10.110.
ps ML

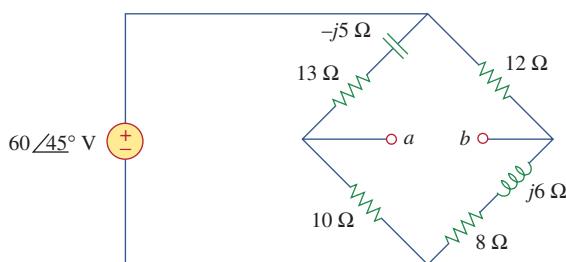**Figure 10.110**

For Prob. 10.67.


- 10.68** Find the Thevenin equivalent at terminals *a-b* in the circuit of Fig. 10.111.
ps ML

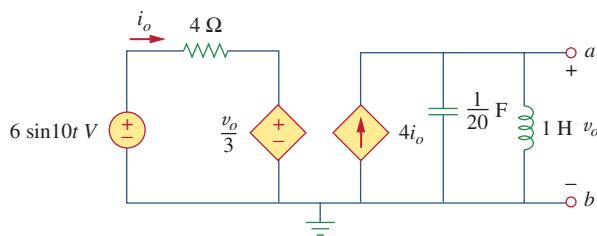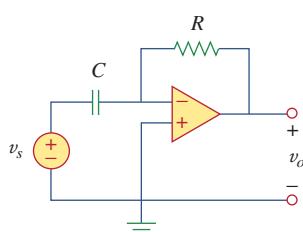**Figure 10.111**

For Prob. 10.68.


Section 10.7 Op Amp AC Circuits

- 10.69** For the differentiator shown in Fig. 10.112, obtain V_o/V_s . Find $v_o(t)$ when $v_s(t) = V_m \sin \omega t$ and $\omega = 1/RC$.

**Figure 10.112**


For Prob. 10.69.

- 10.70** Using Fig. 10.113, design a problem to help other **e2d** students better understand op amps in AC circuits.

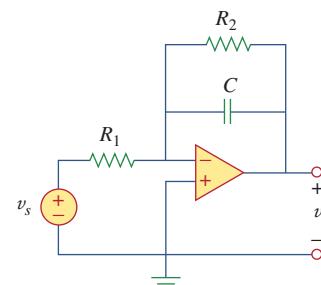**Figure 10.113**


For Prob. 10.70.

- 10.71** Find v_o in the op amp circuit of Fig. 10.114.

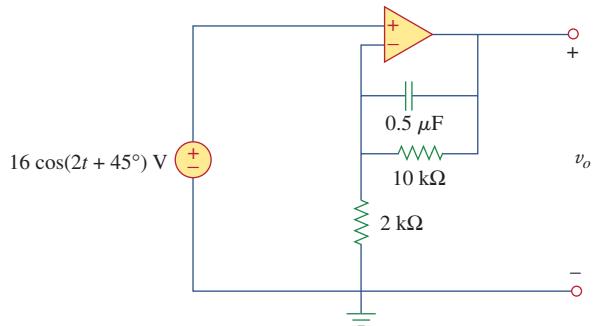**Figure 10.114**


For Prob. 10.71.

- 10.72** Compute $i_o(t)$ in the op amp circuit in Fig. 10.115 if $v_s = 10 \cos(10^4 t + 30^\circ)$ V.

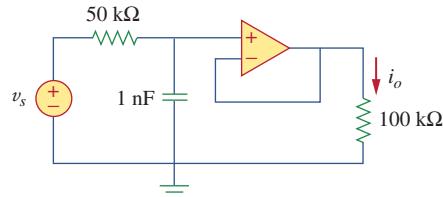
**Figure 10.115**

For Prob. 10.72.

- 10.73** If the input impedance is defined as $Z_{in} = V_s/I_s$, find the input impedance of the op amp circuit in Fig. 10.116 when $R_1 = 10 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, $C_1 = 10 \text{ nF}$, $C_2 = 20 \text{ nF}$, and $\omega = 5000 \text{ rad/s}$.

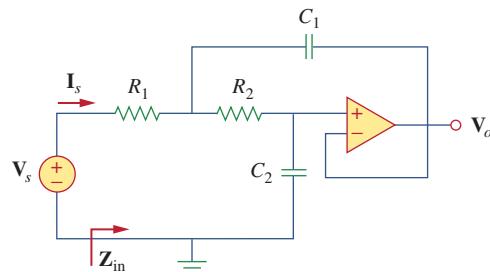**Figure 10.116**


For Prob. 10.73.

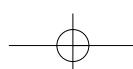

452


Chapter 10 Sinusoidal Steady-State Analysis

- 10.74** Evaluate the voltage gain $A_v = V_o/V_s$ in the op amp circuit of Fig. 10.117. Find A_v at $\omega = 0$, $\omega \rightarrow \infty$, $\omega = 1/R_1C_1$, and $\omega = 1/R_2C_2$.

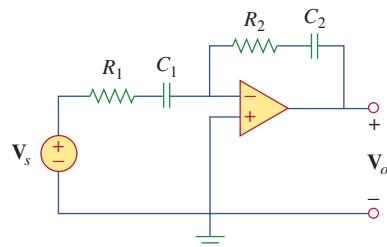**Figure 10.117**


For Prob. 10.74.

- 10.76** Determine V_o and I_o in the op amp circuit of Fig. 10.119. 

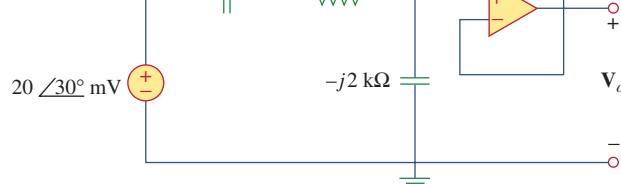**Figure 10.119**


For Prob. 10.76.

- 10.75** In the op amp circuit of Fig. 10.118, find the closed-loop gain and phase shift of the output voltage with respect to the input voltage if $C_1 = C_2 = 1 \text{ nF}$, $R_1 = R_2 = 100 \text{ k}\Omega$, $R_3 = 20 \text{ k}\Omega$, $R_4 = 40 \text{ k}\Omega$, and $\omega = 2000 \text{ rad/s}$. 

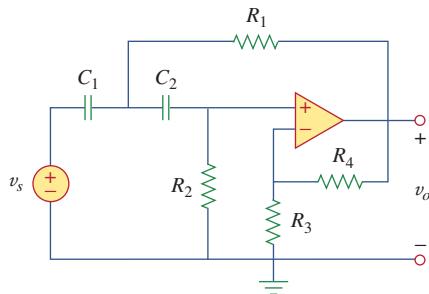**Figure 10.118**


For Prob. 10.75.

- 10.77** Compute the closed-loop gain V_o/V_s for the op amp circuit of Fig. 10.120. 

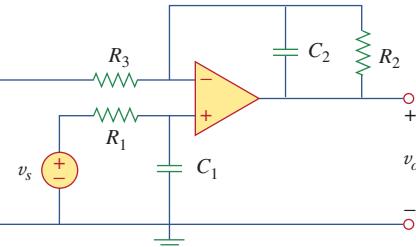
**Figure 10.120**

For Prob. 10.77.

- 10.78** Determine $v_o(t)$ in the op amp circuit in Fig. 10.121 below. 

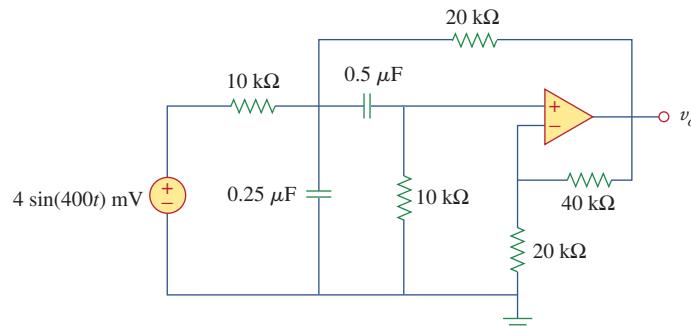**Figure 10.121**

For Prob. 10.78.

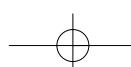

10.79 For the op amp circuit in Fig. 10.122, obtain $v_o(t)$.

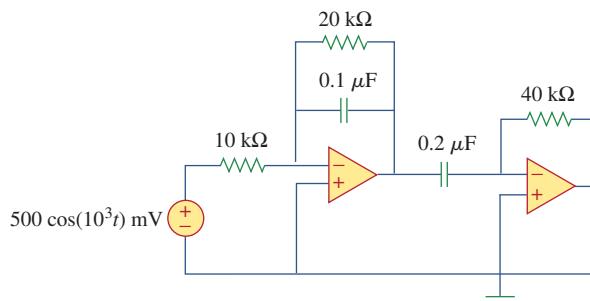


Figure 10.122

For Prob. 10.79.

10.80 Obtain $v_o(t)$ for the op amp circuit in Fig. 10.123 if $v_s = 4 \cos(1000t - 60^\circ)$ V.

ps ML

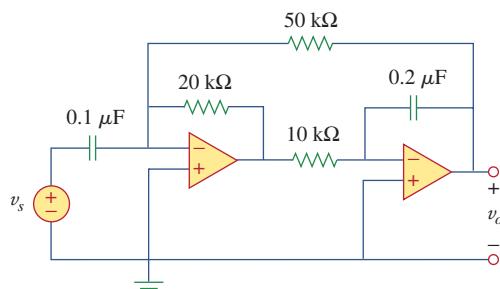


Figure 10.123

For Prob. 10.80.

Section 10.8 AC Analysis Using PSpice

ps

10.81 Use PSpice to determine \mathbf{V}_o in the circuit of Fig. 10.124. Assume $\omega = 1$ rad/s.

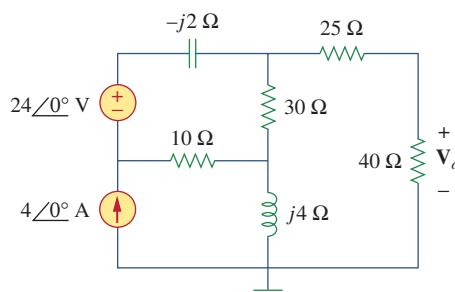


Figure 10.124

For Prob. 10.81.

10.82 Solve Prob. 10.19 using PSpice.

10.83 Use PSpice to find $v_o(t)$ in the circuit of Fig. 10.125. Let $i_s = 2 \cos(10^3 t)$ A.

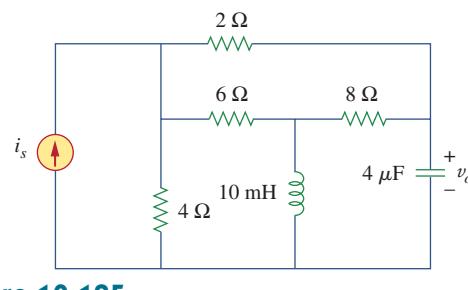


Figure 10.125

For Prob. 10.83.

10.84 Obtain \mathbf{V}_o in the circuit of Fig. 10.126 using PSpice.

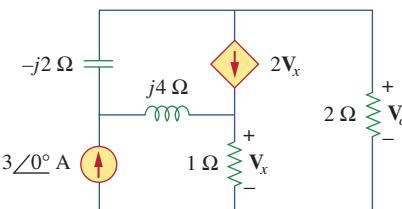


Figure 10.126

For Prob. 10.84.

10.85 Using Fig. 10.127, design a problem to help other **e2d** students better understand performing AC analysis with PSpice.

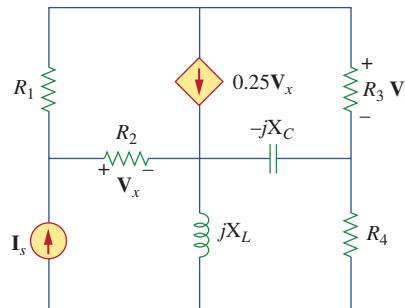


Figure 10.127

For Prob. 10.85.

10.86 Use PSpice to find \mathbf{V}_1 , \mathbf{V}_2 , and \mathbf{V}_3 in the network of Fig. 10.128.


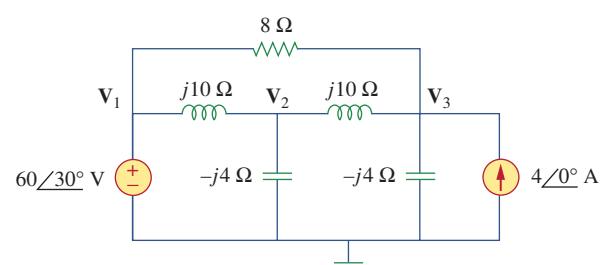
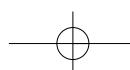


Figure 10.128

For Prob. 10.86.

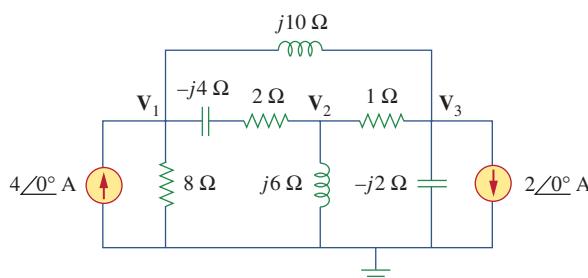


- 10.87** Determine \mathbf{V}_1 , \mathbf{V}_2 , and \mathbf{V}_3 in the circuit of Fig. 10.129 using PSpice.

**Figure 10.129**

For Prob. 10.87.

- 10.88** Use PSpice to find v_o and i_o in the circuit of Fig. 10.130 below.

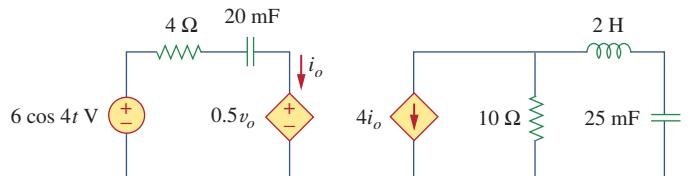**Figure 10.130**

For Prob. 10.88.


Section 10.9 Applications

- 10.89** The op amp circuit in Fig. 10.131 is called an *inductance simulator*. Show that the input impedance is given by

$$Z_{in} = \frac{V_{in}}{I_{in}} = j\omega L_{eq}$$


where

$$L_{eq} = \frac{R_1 R_3 R_4}{R_2} C$$

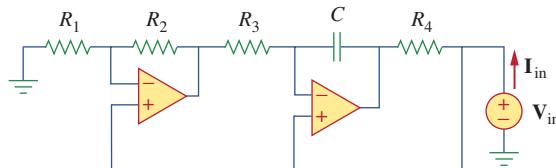**Figure 10.131**

For Prob. 10.89.


- 10.90** Figure 10.132 shows a Wien-bridge network. Show that the frequency at which the phase shift between the input and output signals is zero is $f = \frac{1}{2}\pi RC$, and that the necessary gain is $A_v = V_o/V_i = 3$ at that frequency.

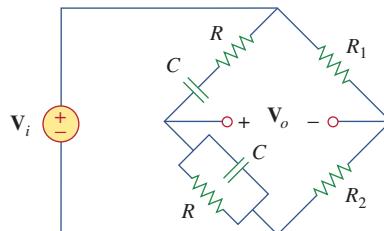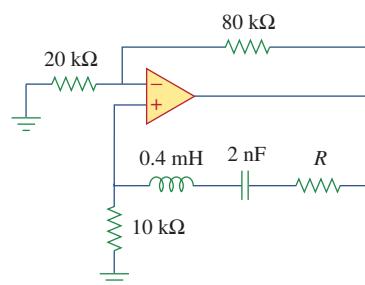**Figure 10.132**


For Prob. 10.90.

- 10.91** Consider the oscillator in Fig. 10.133.

- Determine the oscillation frequency.
- Obtain the minimum value of R for which oscillation takes place.


**Figure 10.133**

For Prob. 10.91.

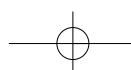

- 10.92** The oscillator circuit in Fig. 10.134 uses an ideal op amp.

- (a) Calculate the minimum value of R_o that will cause oscillation to occur.
 (b) Find the frequency of oscillation.

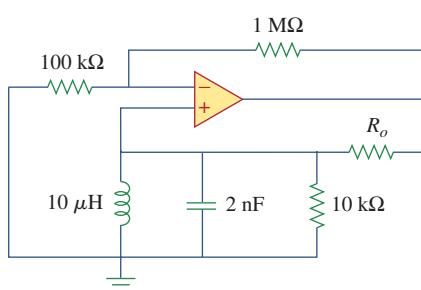
**Figure 10.134**

For Prob. 10.92.

- 10.93** Figure 10.135 shows a *Colpitts oscillator*. Show that
e2d the oscillation frequency is

$$f_o = \frac{1}{2\pi\sqrt{LC_T}}$$

where $C_T = C_1C_2/(C_1 + C_2)$. Assume $R_i \gg X_{C_2}$.

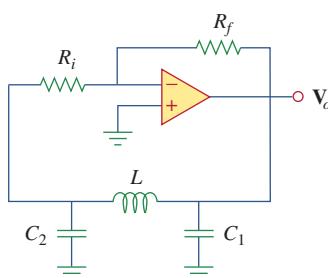**Figure 10.135**


A Colpitts oscillator; for Prob. 10.93.

(Hint: Set the imaginary part of the impedance in the feedback circuit equal to zero.)

- 10.94** Design a Colpitts oscillator that will operate at 50 kHz.
e2d

- 10.95** Figure 10.136 shows a *Hartley oscillator*. Show that the frequency of oscillation is

$$f_o = \frac{1}{2\pi\sqrt{C(L_1 + L_2)}}$$

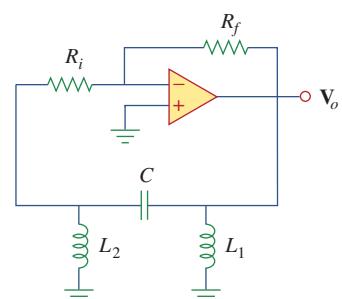**Figure 10.136**

A Hartley oscillator; for Prob. 10.95.


- 10.96** Refer to the oscillator in Fig. 10.137.

- (a) Show that

$$\frac{V_2}{V_o} = \frac{1}{3 + j(\omega L/R - R/\omega L)}$$

- (b) Determine the oscillation frequency f_o .

- (c) Obtain the relationship between R_1 and R_2 in order for oscillation to occur.

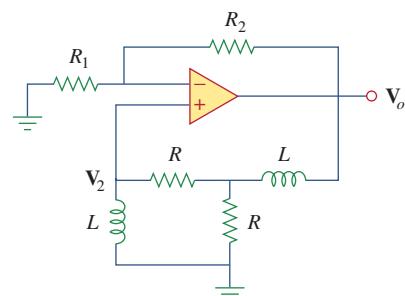**Figure 10.137**

For Prob. 10.96.